表1.1 电流表外接	120Ω	正向						表1.2 电流	<b>流表外接</b>	120Ω	反向									
给定电压(V)	0	2	4	6	8	10		给定电压(V)		0	2	4	6	8	10					
测量电压(V)	0	1.93	3.85	5.82	7.8	9.71		测量电压 (V)		0	1.97	3.95	5.92	7.9	9.88					
测量电流 (mA)	0	16.36	32.7	49.58	66.68	83.46		测量电流(mA)		0	16.87	33.8	50.81	67.93	84.95					
计算电阻(Ω)	\	117.9707	117.737	117.386	116.9766	116.3432		计算电阻 (Ω)		١	116.7753	116.8639	116.5125	116.2962	116.3037		-1			
			•	•			•			•	•	•								
表2.1 电流表外接	120Ω	正向						表2.2 电流		120Ω	反向									
给定电流(mA)	0	17	37	57	77	97		给定电流	(mA)	0	17	37	57	77	97					
测量电压(V)	0	2.05	4.39	6.75	9.09	11.37		测量电压(V)		0	2.03	4.34	6.67	9	11.33					
测量电流(mA)	0	17.45	37.31	57.41	77.57	97.37		测量电流 (mA)		0	17.42	37.25	57.29	77.4	97.35					
计算电阻 (Ω)	\	117.4785	117.6628	117.5753	117.1845	116.7711		计算电阻 (Ω)		\	116.5327	116.5101	116.4252	116.2791	116.3842					
			-							-		-	-							
表3.1 电压表外接	120Ω	正向					_	表3.2 电压		120Ω	反向									
给定电压 (V)	0	2	4	6	8	10		给定电压 (V)		0	2	4	6	8	10					
测量电压(V)	0	2	4	6	8	10		测量电压(V)		0	2	4	6	8	10					
测量电流(mA)	0	15.87	32.32	49.06	66.08	83.26		测量电流(mA)		0	16.66	33.36	50.08	66.77	83.36					
计算电阻 (Ω)	\	126.0239	123.7624	122.2992	121.0654	120.1057		计算电阻 (Ω)		\	120.048	119.9041	119.8083	119.8143	119.9616					
表4.1 电压表外接	120Ω						,	表4.2 电/		120Ω	反向									
给定电流(mA)	0	17	37	57	77	97		给定电流 (mA)		0	17	37	57	77	97					
测量电压(V)	0	2.08	4.43	6.81	9.19	11.51		测量电压 (V)		0	2.11	4.51	6.92	9.32	11.58					
测量电流(mA)	0	17.43	37.26	57.33	77.48	97.23		测量电流 (mA)		0	17.51	37.37	57.43	77.59	97.26					
计算电阻 (Ω)	\	119.3345	118.8943	118.786	118.6113	118.3791		计算电阻 (Ω)		\	120.5026	120.685	120.4945	120.1186	119.0623					
±54 + > ± 4 +>		<b>T</b> (-																		
表5.1 电流表外接 给定电压(V)	D3	正向	0.05	I 0.4	0.45		0.50	1 054 1	0.50	0.50	I 00	0.00	1 004	0.00	0.00	0.7	0.70	0.70	0.74	1 0 70
147-07-17	0	0.3	0.35	0.4	0.45	0.48	0.52	0.54	0.56	0.58	0.6	0.62	0.64	0.68	0.69	0.7	0.72	0.73	0.74	0.76
测量电流(mA)	0	0.002	0.008	0.028	0.096	0.194	0.466	0.7	1.056	1.58	2.32	3.445	5.147	10.342	12.412	14.434	19.64	22.446	25.7	32.8
表5.2 电流表外接	D.0																			
会定电压(V)	D3	<u> </u>	1 1	<u> </u>	T 4	T C		1												
测量电流(MA)	0	0.003	0.003	0.003	0.004	0.005	0.005	1												
州里电流 (MA)	U	0.003	0.003	0.003	0.004	0.005	0.005	]												
表6.1 电流表外接	D4	正向																		
给定电压(V)	D4 0	<u> </u>	1.5	1.9	2	2.11	2.16	2.27	2.38	2.46	2.64	2.85	3	1						
测量电流(mA)	0	1.00E-04	0.003	0.084	0.152	0.252	0.409	0.551	0.65	0.77	0.902	2.85	1.247	1						
/对里七/// (IIIA)	U	1.00E-04	0.003	0.004	0.132	0.232	0.409	0.551	0.00	0.11	0.902	1.1	1.241	J						
表6.2 电流表外接	D4	反向																		
给定电压(V)	0	2	4	6	8	10	12	1												
测量电流(mA)	0	0.002	0.002	0.002	0.002	0.003	0.003	†												
"3 = 0 // (···/ )		0.002	0.002	0.002	0.002	0.000	0.000	1												